



Finite state machines

Использование

- Любые системы с последовательными переходами
- Интерфейсы
- Тестирование




Описание графом переходов

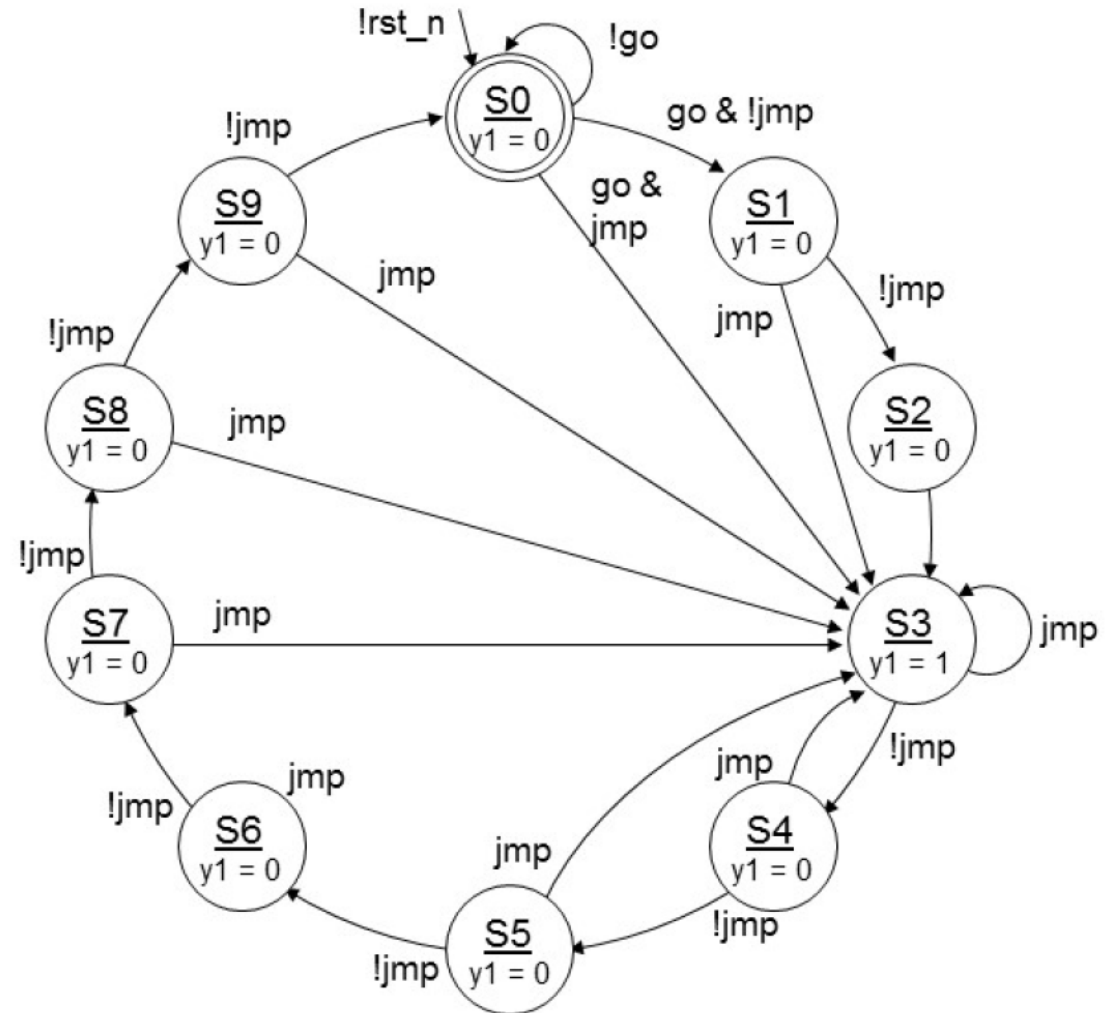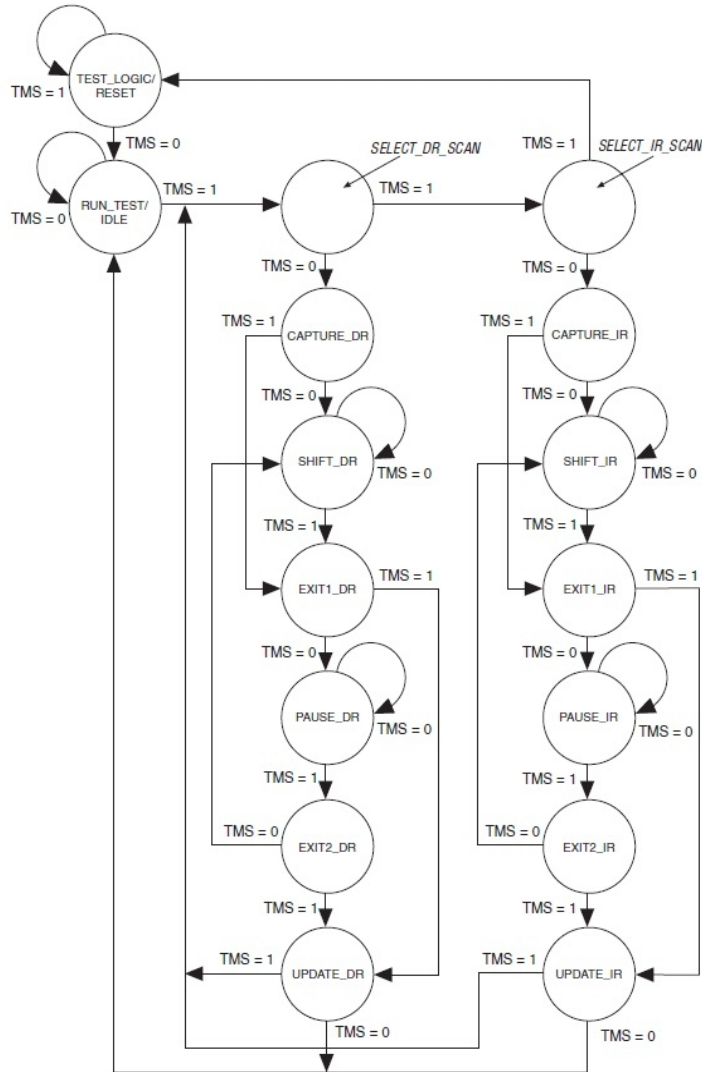


Moore type

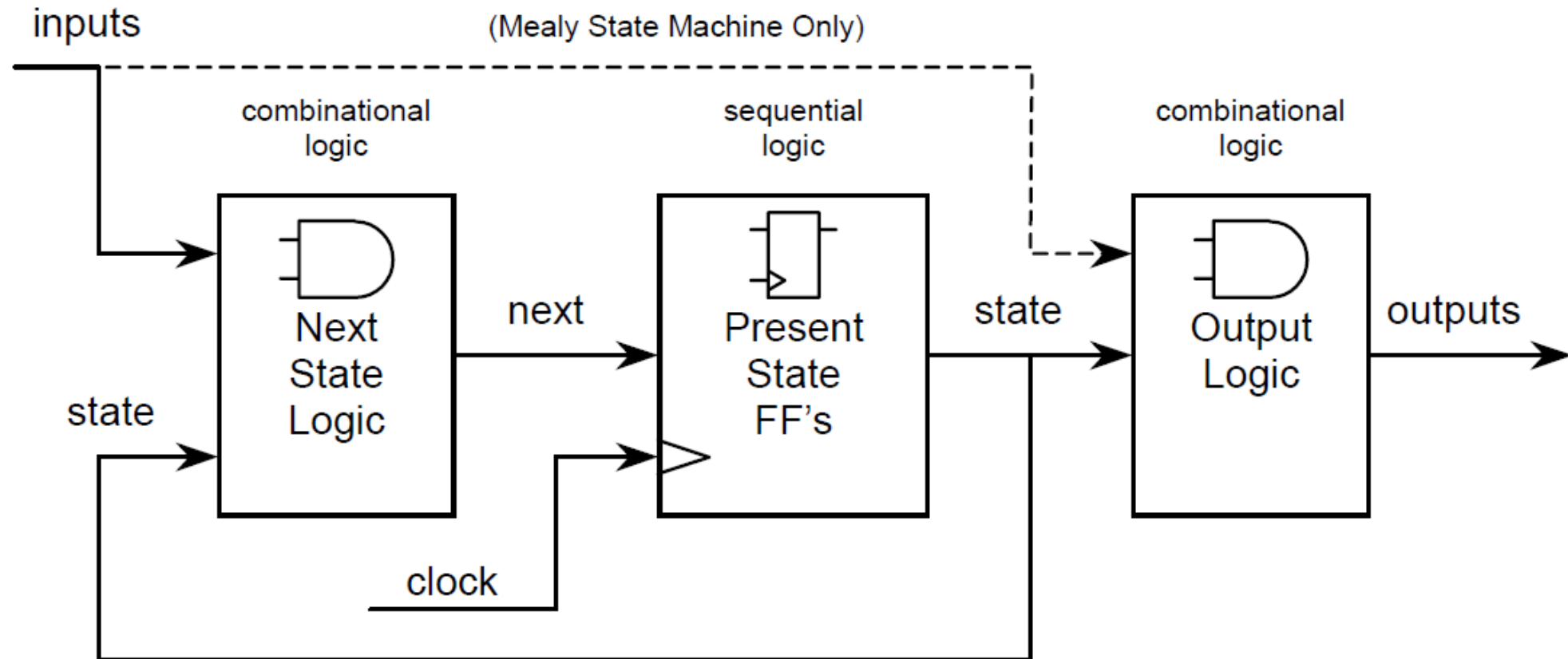- Выходы есть функции только текущего состояния
- Есть целый такт на распространение сигнала по комбинационному пути




Mealy type

 - Часть выходов есть функции только текущего состояния и часть выходов есть функции входов
- Есть условия на тайминг входных сигналов



One always block with registered outputs

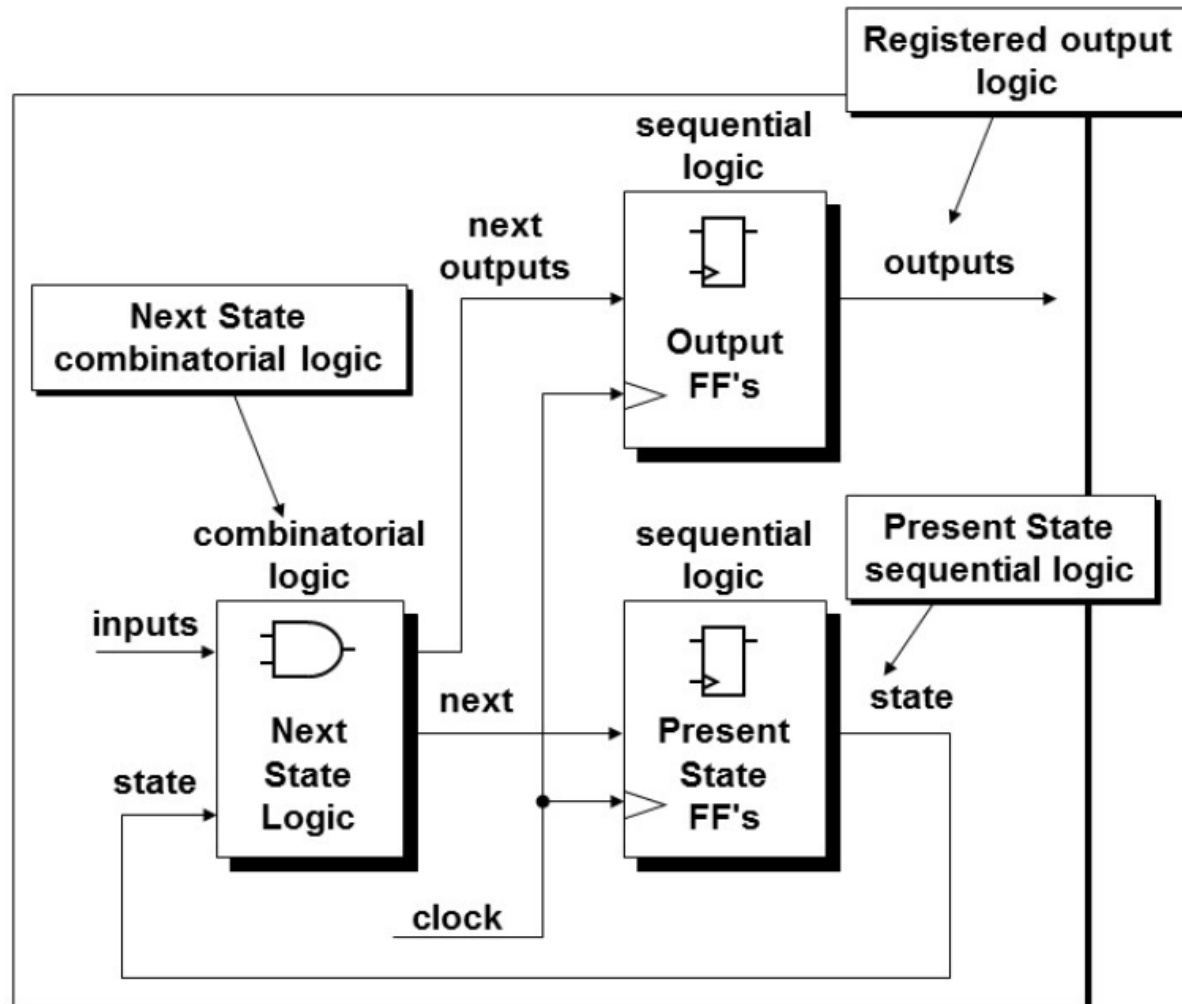

```
module fsm
  (... ports ...);
  import fsm_pkg::*;
  state_e state;
```

```
always_ff @(posedge clk, negedge rst_n)
  if (!rst_n) begin
    state <= IDLE;
    <outputs> <= '0;
  end
  else begin
    state <= XXX;
    <outputs> <= '0;
    case (state)
      IDLE : if (go) begin
              rd <= '1;
            end
            else
      READ : begin
              rd <= '1;
            end
            ...
          endcase
    end
```

**Present state
being registered**


**Next outputs
being registered**

state <= READ;
state <= IDLE;
state <= DLY;

**Next states
being registered**

```
endmodule
```


Two always blocks, combinational outputs

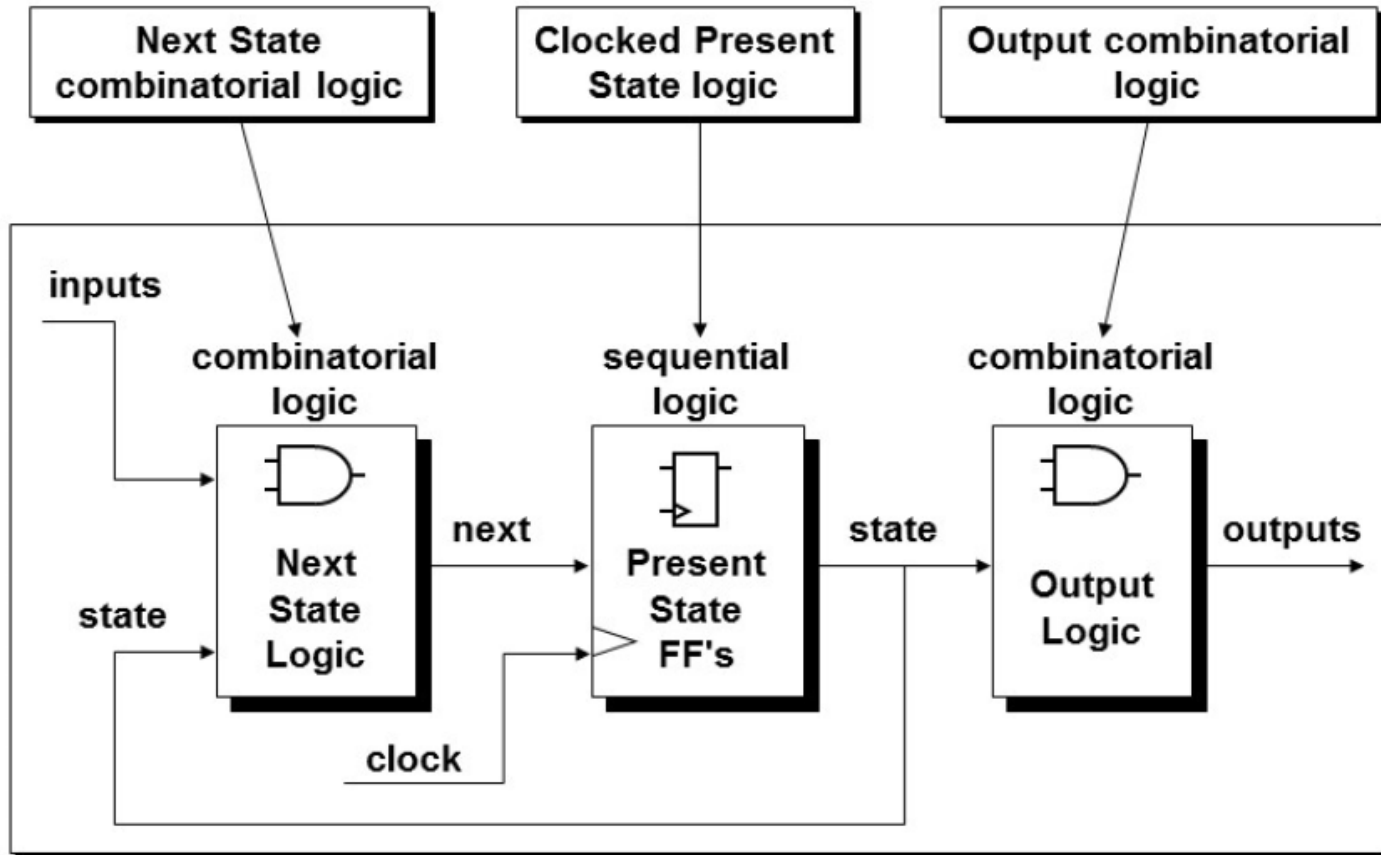

```
module fsm
  (... ports ...);
  import fsm_pkg::*;
  state_e state, next;


  always_ff @(posedge clk or negedge rst_n)
    if (!rst_n) state <= IDLE;
    else state <= next;

  always_comb begin
    next = XXX;
    rd = '0;
    ds = '0;
    case (state)
      IDLE : if (go)      next = READ;
              else       next = IDLE;
      READ : begin
                  rd = '1;
                  next = DLY;
              end
      ...
    endcase
  end
endmodule
```

Clocked present state logic

Next & output combinational logic

Three always blocks, registered outputs

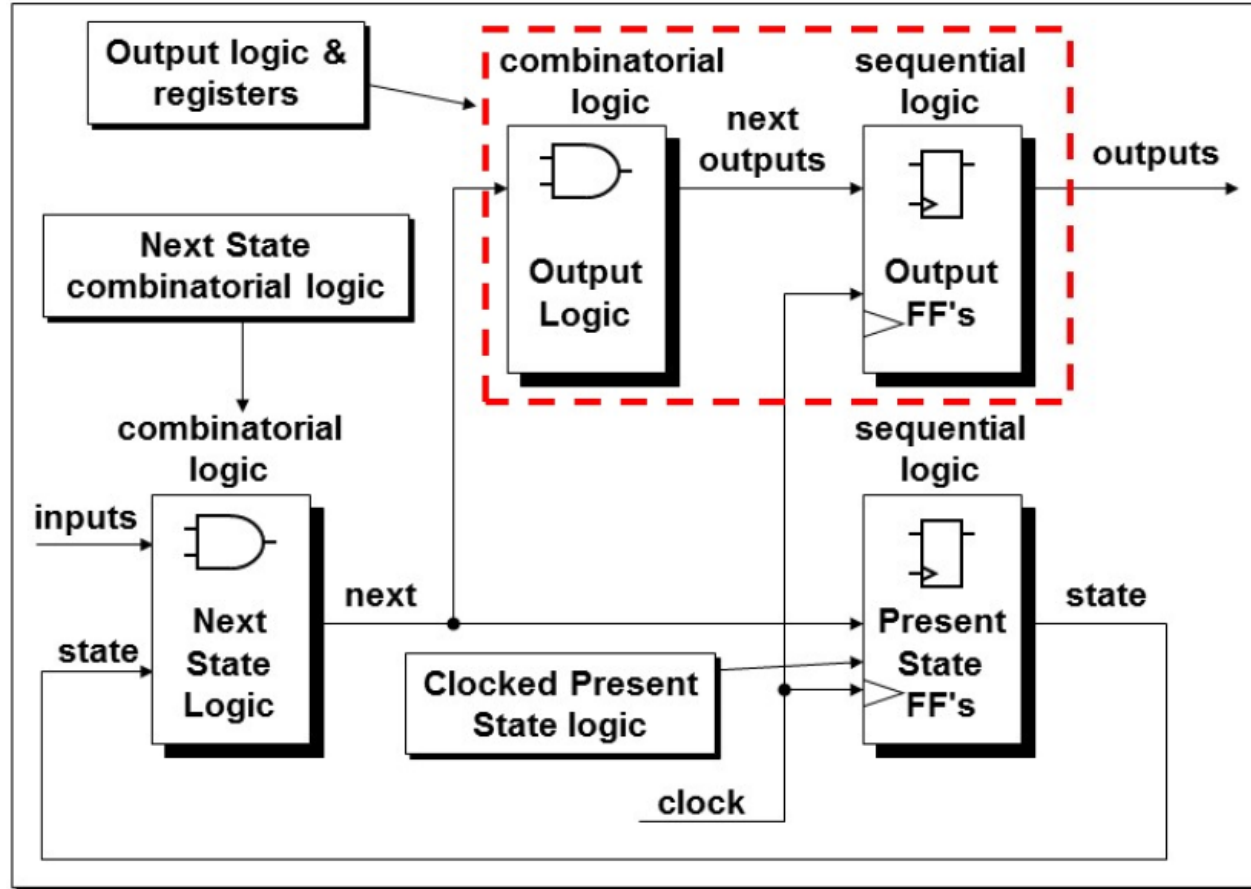

```

module fsm
  (... ports ...);
  import fsm_pkg::*;
  state_e state, next;

  always_ff @(posedge clk or negedge rst_n)
    if (!rst_n) state <= IDLE;
    else state <= next;

  always_comb begin
    next = XXX;
    case (state)
      IDLE : if (go) next = READ;
              else next = IDLE;
      READ : next = DLY;
      ...
    endcase
  end

  always_ff @(posedge clk or negedge rst_n)
    if (!rst_n) begin
      rd <= '0;
      ds <= '0;
    end
    else begin
      rd <= '0;
      ds <= '0;
      case (next)
        READ : rd <= '1;
        ...
      endcase
    end
  end
endmodule

```


Clocked present state logic

always_comb next logic

always_ff next-output logic & registers

When next is READ, output will be rd<=1

Four always blocks, registered

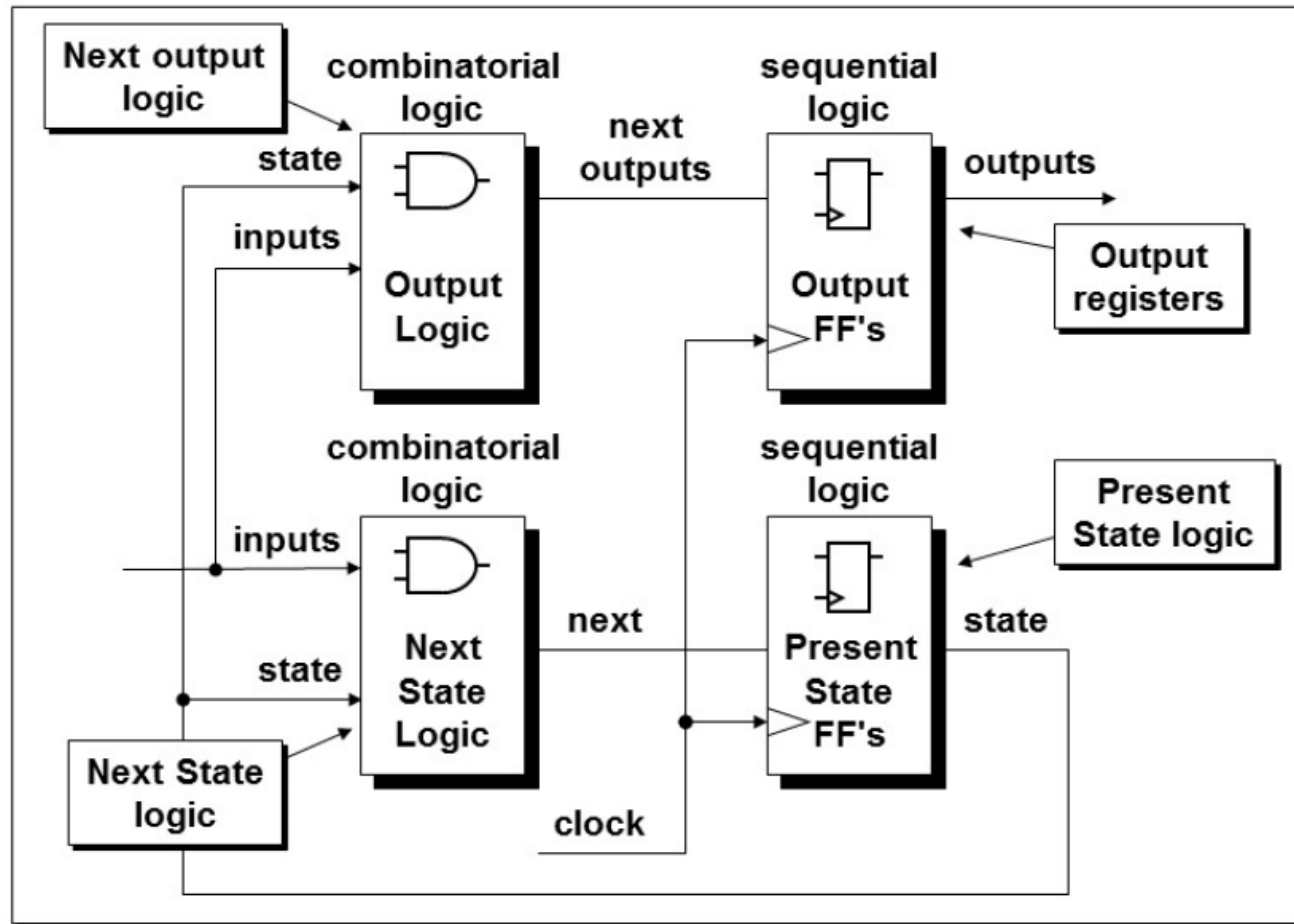

```

module fsm
  (... ports ...);
  import fsm_pkg::*;
  state_e state, next;

  always_ff @(posedge clk or negedge rst_n)
    if (!rst_n) state <= IDLE;
    else      state <= next;

  always_comb begin
    next = XXX;
    case (state)
      IDLE : if (go)  next = READ;
              else   next = IDLE;
      ...
    endcase
  end

  always_comb begin
    n_rd = '0;
    n_ds = '0;
    case (state)
      READ : n_rd = '1; // READ
      ...
    endcase
  end

  always_ff @(posedge clk or negedge rst_n)
    if (!rst_n) begin ...
    else begin
      rd <= n_rd;
      ds <= n_ds;
    end
  end
endmodule

```

Clocked present state logic

always_comb next logic


always_comb next-output logic

next-outputs

always_ff output registers


Binary vs OneHot encoding

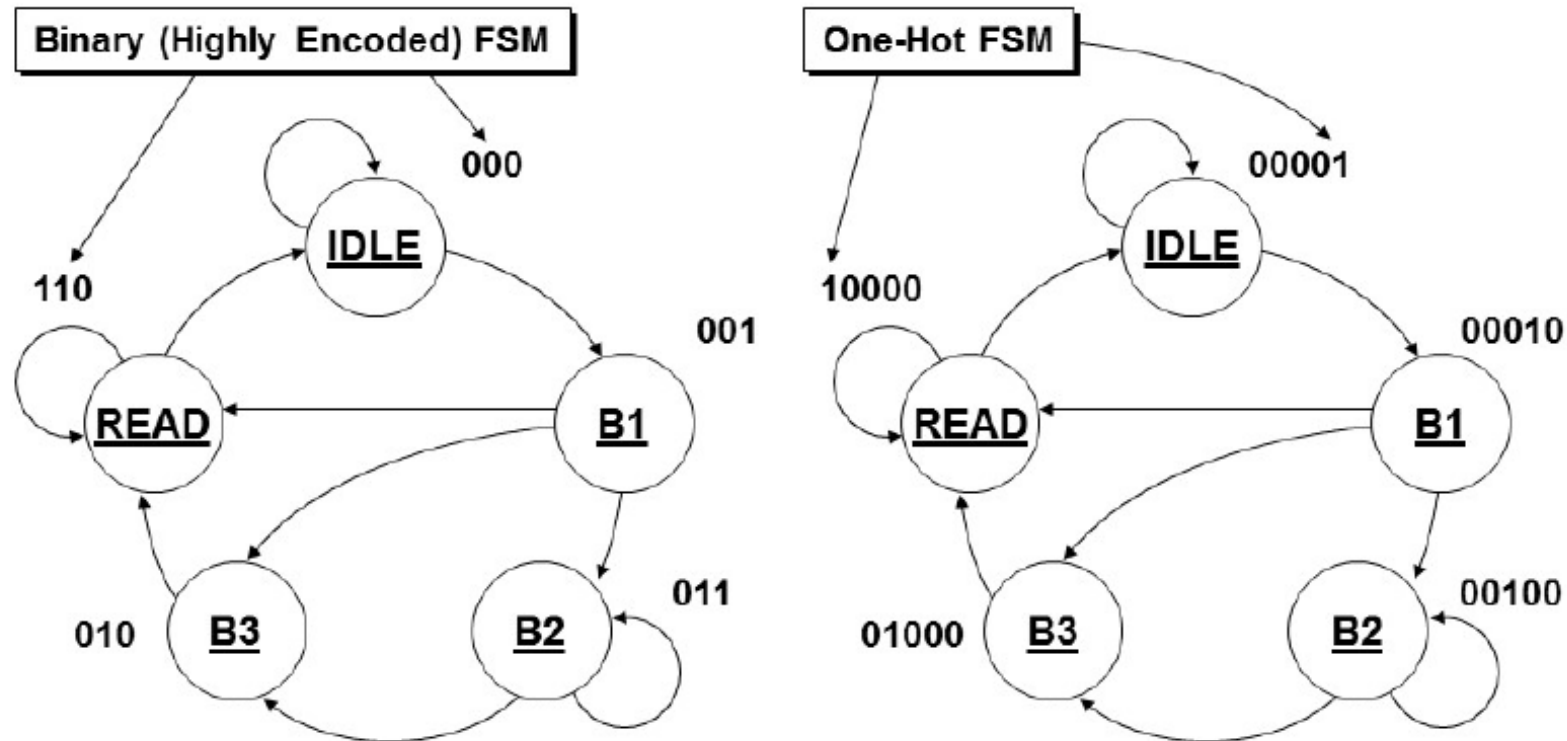- One-hot быстрее переключается между состояниями, но требует больше всего триггеров



ASIC -vs- FPGA Synthesis

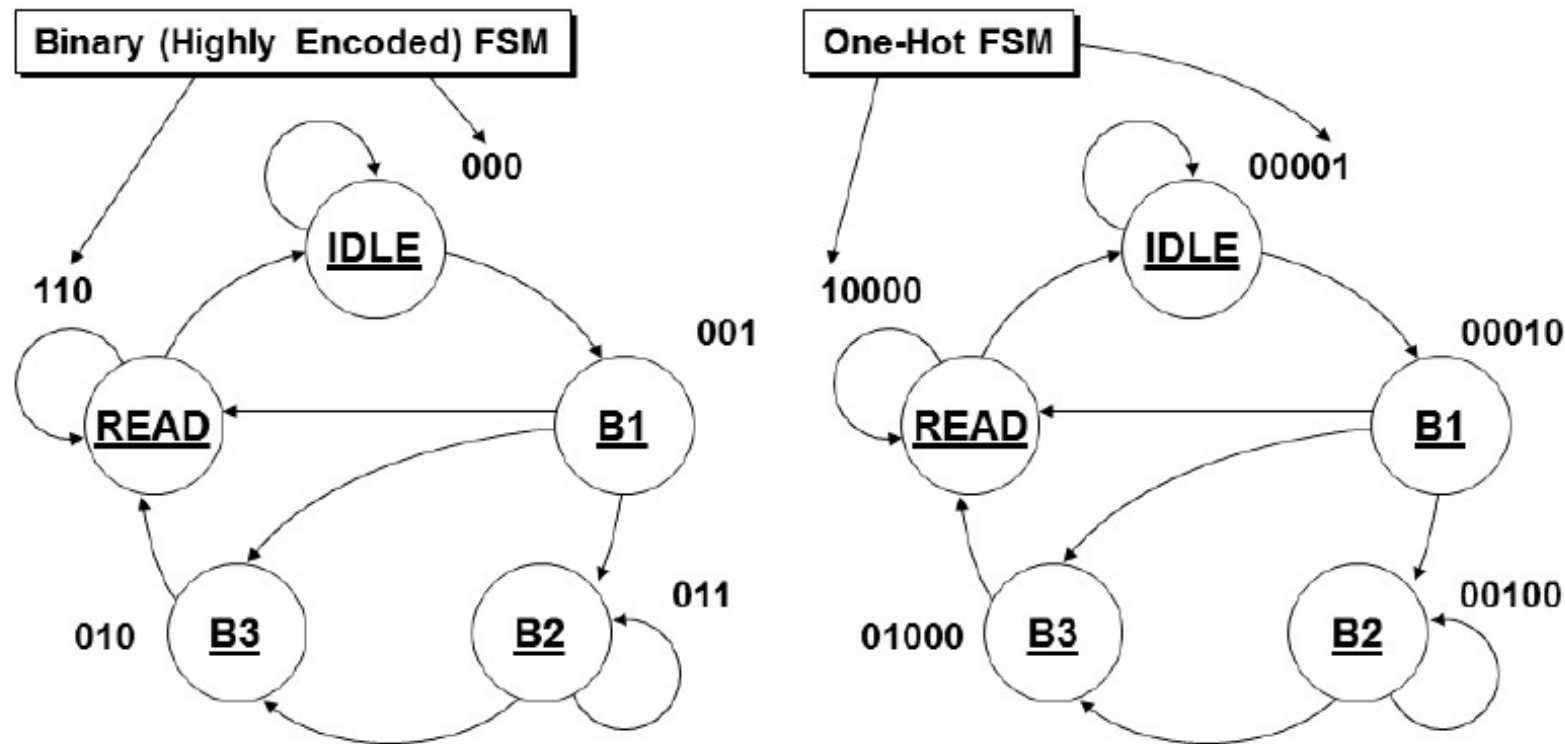- ASIC: “больше” комбинационных элементов
- FPGA: “больше” последовательных элементов



Code style and safety

- localparam
- case, casex, casez
- default state
- All zero, all ones, all x

```
data[15:0] = {'1', 4'hA, '0};  
// is equal to 16'b0000_0000_0011_0100 or 16'h0034  
data[15:0] = {'0', '1', '0};  
// is equal to 16'b0000_0000_0000_0010 or 16'h0002
```

- Use XXX state to debug

FSM state register

```
always_ff @(posedge clk, negedge rst_n)
    if (!rst_n) state <= IDLE;
    else          state <= next;
```


```
always_ff @(posedge clk, negedge rst_n) begin
    testbad <= go;
    if (!rst_n) state <= IDLE;
    else          state <= next;
end
```

Use pre-default-x

- Ошибка в случае потери состояния
- Явное переключение состояния
- Лучше результаты синтеза

```
always_comb begin
    next = XXX;                // Pre-default-X assignment
    case (state)
        IDLE : if (go)    next = READ;
                else      next = IDLE; //@ loopback
        READ :           next = DLY;
        DLY  : if (!ws)   next = DONE;
                else      next = READ;
        DONE :           next = IDLE;
        default:         next = XXX;  // case-default-X assignment
    endcase
end
```


Пример

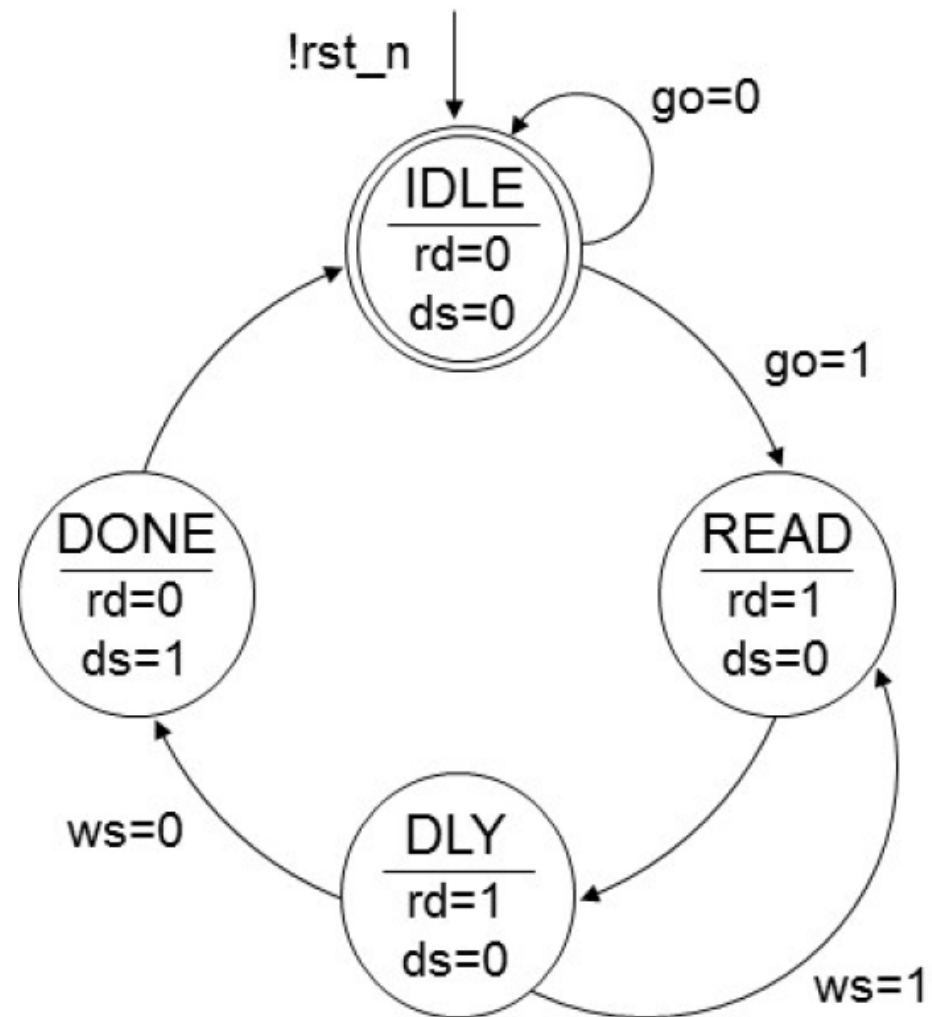

Пример

```
always_ff @(posedge clk, negedge rst_n)
  if (!rst_n) begin
    state <= IDLE;
    rd    <= '0;
    ds    <= '0;
  end
  else begin
    state <= XXX;           //@ LB
    rd    <= '0;
    ds    <= '0;
    case (state)
      IDLE : if (go) begin
                rd <= '1;
                state <= READ;
              end
            else
                state <= IDLE; //@ LB
      READ  : begin
                rd <= '1;
                state <= DLY;
              end
    end
  end
```

```
      DLY   : if (!ws) begin
                ds <= '1;
                state <= DONE;
              end
            else begin
                rd <= '1;
                state <= READ;
              end
      DONE  :
      default: begin
                ds <= 'x;
                rd <= 'x;
                state <= XXX;
              end
    endcase
  end
```

Пример

```
always_ff @(posedge clk, negedge rst_n)
    if (!rst_n) state <= IDLE;
    else          state <= next;

always_comb begin
    next = XXX;          //@LB next = state;
    rd   = '0;
    ds   = '0;
    case (state)
        IDLE : if (go)      next = READ;
                else        next = IDLE; //@ LB
        READ : begin
                    rd = '1;
                    next = DLY;
                end
    end
```

```
        DLY : begin
                    rd = '1;
                    if (!ws) next = DONE;
                    else     next = READ;
                end
        DONE : begin
                    ds = '1;
                    next = IDLE;
                end
        default: begin
                    ds = 'x;
                    rd = 'x;
                    next = XXX;
                end
    endcase
end
```

Пример

```
always_ff @(posedge clk, negedge rst_n)
    if (!rst_n) state <= IDLE;
    else          state <= next;

always_comb begin
    next = XXX;          //@LB next = state;
    case (state)
        IDLE : if (go)    next = READ;
                else      next = IDLE; //@ LB
        READ :            next = DLY;
        DLY  : if (!ws) next = DONE;
                else      next = READ;
        DONE :            next = IDLE;
        default:          next = XXX;
    endcase
end
```

```
always_ff @(posedge clk, negedge rst_n)
    if (!rst_n) begin
        rd <= '0;
        ds <= '0;
    end
    else begin
        rd <= '0;
        ds <= '0;
        case (next)
            IDLE : ;
            READ : rd <= '1;
            DLY  : rd <= '1;
            DONE : ds <= '1;
            default: {rd,ds} <= 'x;
        endcase
    end
```

Пример

```
always_ff @(posedge clk, negedge rst_n)
  if (!rst_n) state <= IDLE;
  else          state <= next;
```

```
always_comb begin
  next = XXX;          //@LB next = state;
  case (state)
    IDLE : if (go)      next = READ;
            else        next = IDLE; //@ LB
    READ  :              next = DLY;
    DLY   : if (!ws)     next = DONE;
            else        next = READ;
    DONE  :              next = IDLE;
    default:             next = XXX;
  endcase
end
```

```
always_comb begin
  n_rd = '0;
  n_ds = '0;
  case (state)
    IDLE : if ( go)      n_rd = '1; // READ
            else ;          // IDLE
    READ  :              n_rd = '1; // DLY
    DLY   : if ( ws)     n_rd = '1; // READ
            else        n_ds = '1; // DONE
    DONE  : ;              // IDLE
    default:             {n_rd,n_ds} = 'x;
  endcase
end
```

```
always_ff @(posedge clk, negedge rst_n)
  if (!rst_n) begin
    rd <= '0;
    ds <= '0;
  end
  else begin
    rd <= n_rd;
    ds <= n_ds;
  end
end
```

Литература

Sunburst Design -
FiniteStateMachine(FSM)Design&SynthesisusingSystemVerilog-PartI